

NS/SS 123

APPLIED PHYSICS


SINGLE LOOP CIRCUITS

- ❖ Polarities: Positive and Negative
- ❖ AC & DC
- ❖ Circuit Elements: Resistors, Capacitors, Inductors
- ❖ Sources: Dependent & Independent
- ❖ Voltage Source, Current Source

Charge Pumping:

- ❖ To maintain the charge flow: emf/potential difference
- ❖ Common emf devices: Generator, solar cell, Batteries
- ❖ Work on Charge carrier and maintains a potential difference


Work, Energy & emf:

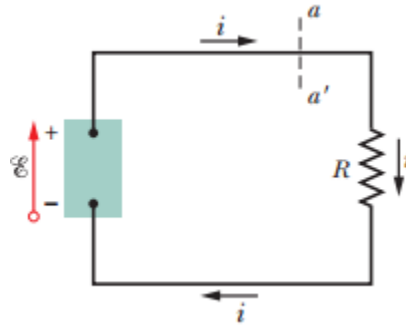

- ❖ No emf, no net charge flow
- ❖ Within emf device: charges flow from negative to positive opposite to electric field (chemicals, mechanical force or light etc)
- ❖ EMF: emf of an device is work per unit charge that a device does moving a charge from its lower potential to higher potential
- ❖ Ideal emf: Potential difference of device terminals is equal to device emf (no internal resistance)
- ❖ Real emf device: when current flows potential difference between terminals differs from device emf
- ❖ Emf device is connected in circuit then energy is transferred to the circuit elements

Calculating Current in Single loop

❖ Energy Method:

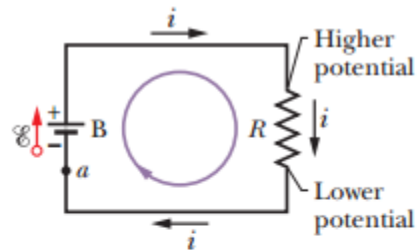


$$dW = \mathcal{E} dq = \mathcal{E} i dt$$

$$\mathcal{E} i dt = i^2 R dt$$


$$\mathcal{E} = iR$$

$$i = \frac{\mathcal{E}}{R}$$

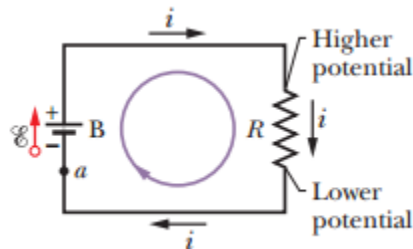
❖ Potential Method: Algebraic sum of changes in potential encountered in complete traversal of any loop of circuit must be zero (KVL)



$$-\mathcal{E} + iR = 0$$

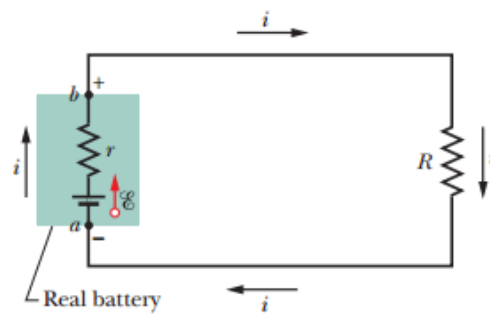

$$i = \frac{\mathcal{E}}{R + r}$$

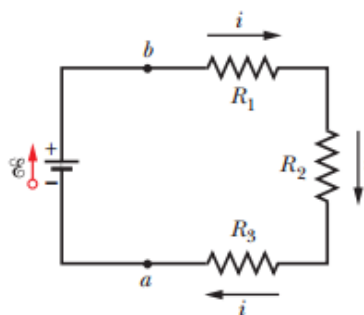



$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$


$$i = \frac{\mathcal{E}}{R_{\text{cq}}}$$


$$R_{\text{cq}} = R_1 + R_2 + R_3$$


$$R_{\text{cq}} = \sum_{j=1}^n R_j$$

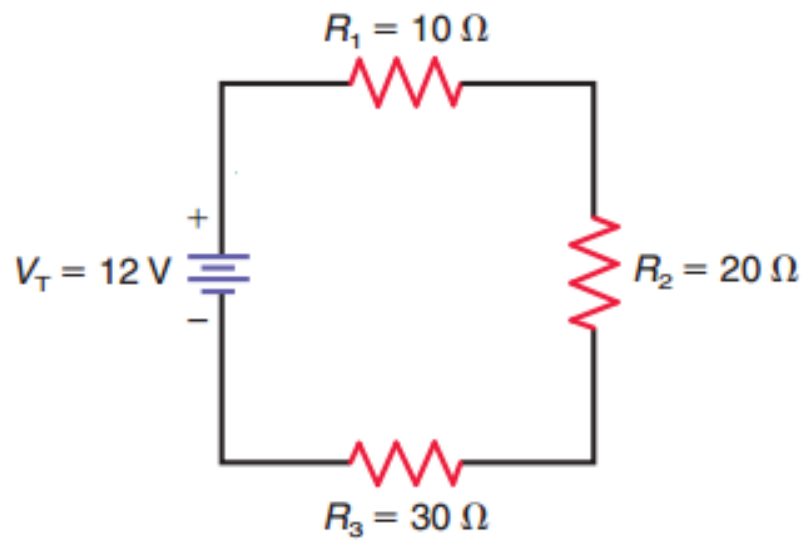


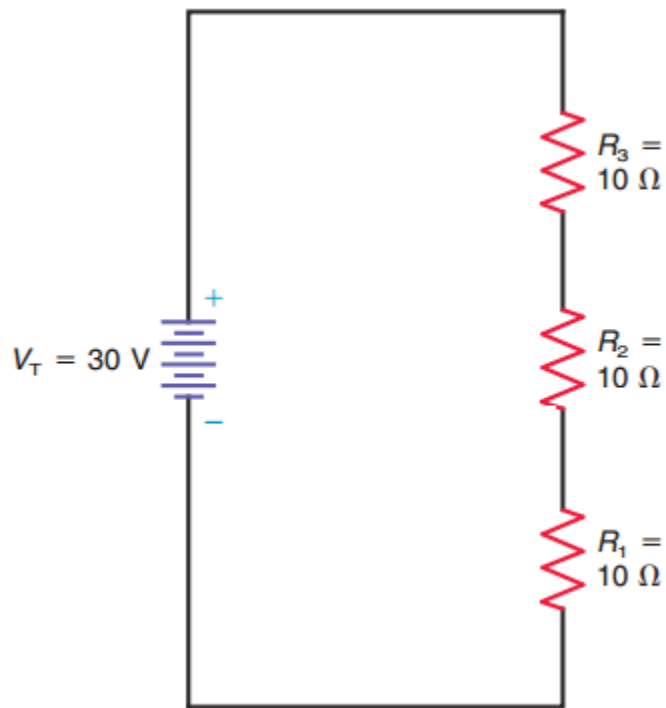


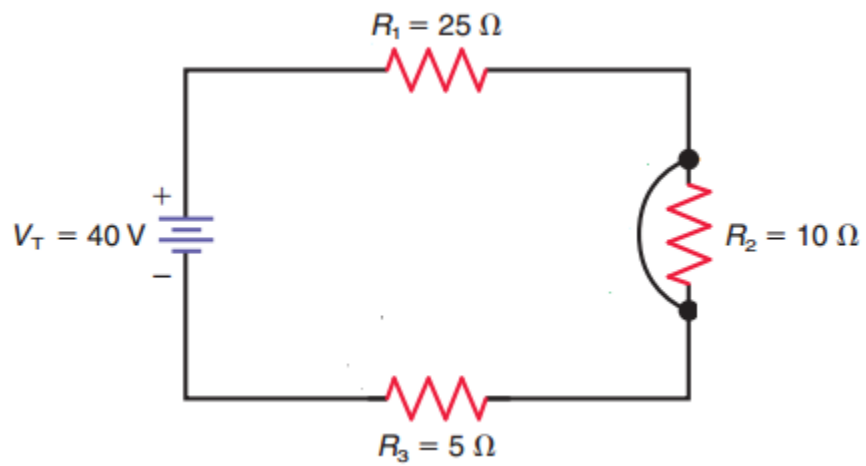


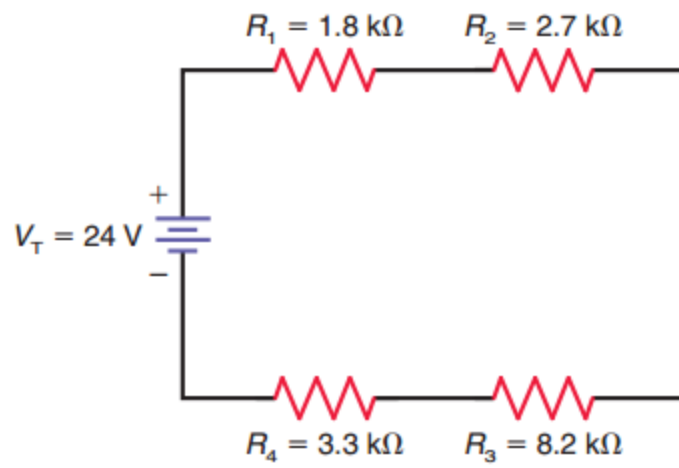

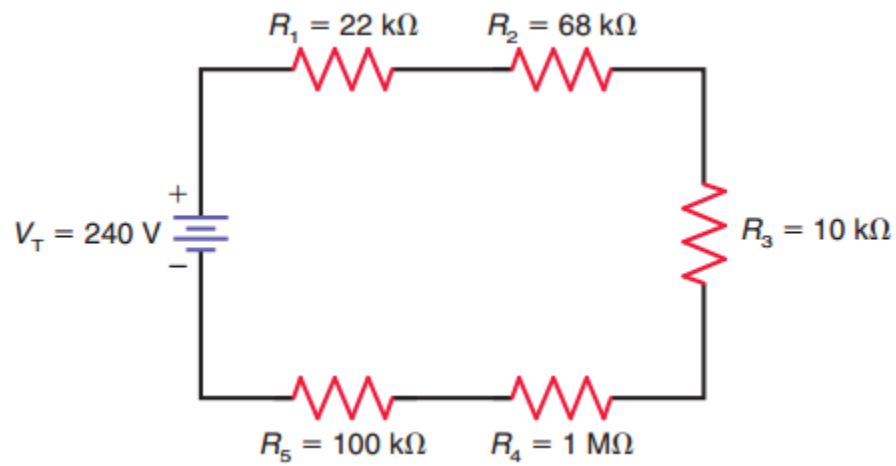


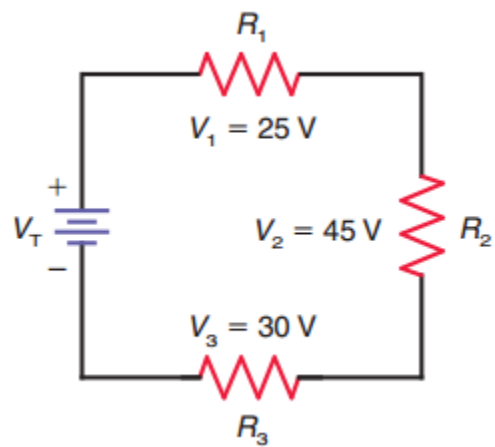

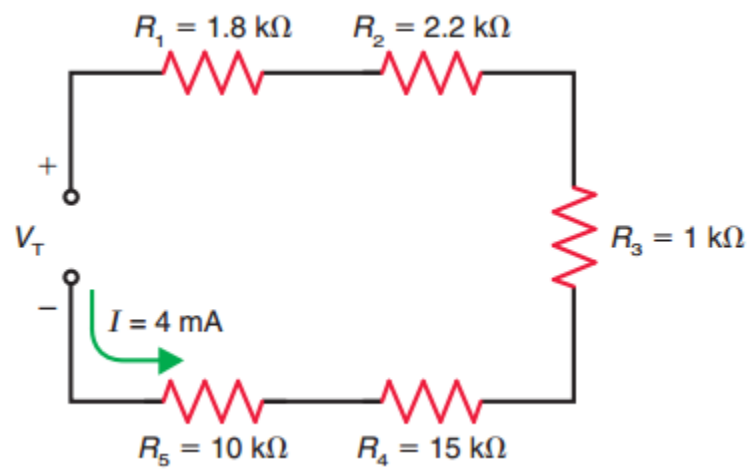

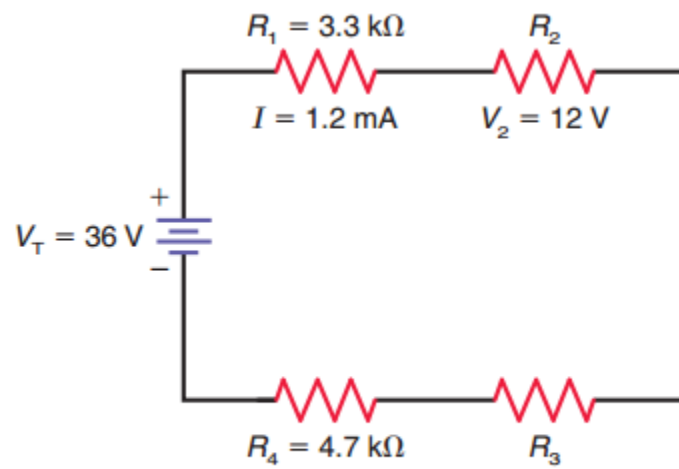

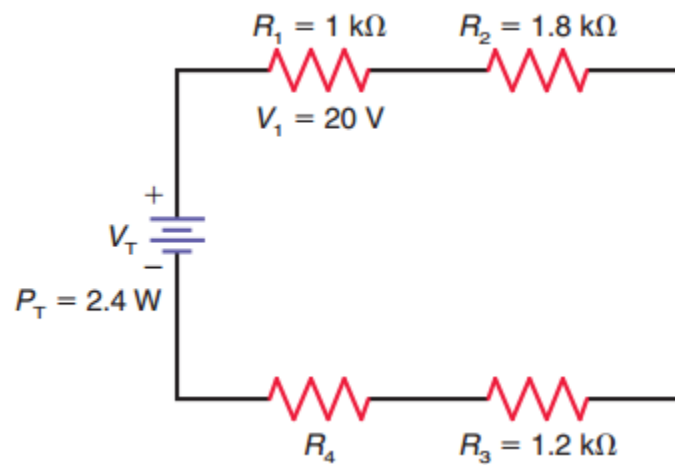$R_T, V_1, V_3, V_4, R_2, R_3, P_T, P_1, P_2, P_3, P_4.$



$I, R_1, V_1, V_2, V_3, V_4, R_4, P_1, P_2, P_3, P_4$

THANK YOU!